



Chapter 32A – AC Circuits

A PowerPoint Presentation by

Paul E. Tippens, Professor of Physics

Southern Polytechnic State University

© 2007

Objectives: After completing this module, you should be able to:

- Describe the sinusoidal variation in **ac current and voltage**, and calculate their **effective** values.
- Write and apply equations for calculating the **inductive and capacitive reactances** for inductors and capacitors in an ac circuit.
- Describe, with diagrams and equations, the **phase relationships** for circuits containing **resistance, capacitance, and inductance**.

Objectives (Cont.)

- Write and apply equations for calculating the **impedance**, the **phase angle**, the **effective current**, the **average power**, and the **resonant frequency** for a series ac circuit.
- Describe the basic operation of a **step-up** and a **step-down transformer**.
- Write and apply the **transformer equation** and determine the **efficiency** of a transformer.


Alternating Currents

An **alternating current** such as that produced by a generator has no direction in the sense that direct current has. The magnitudes vary **sinusoidally** with time as given by:

AC-voltage
and current


$$\mathcal{E} = \mathcal{E}_{\max} \sin \theta$$

$$i = i_{\max} \sin \theta$$

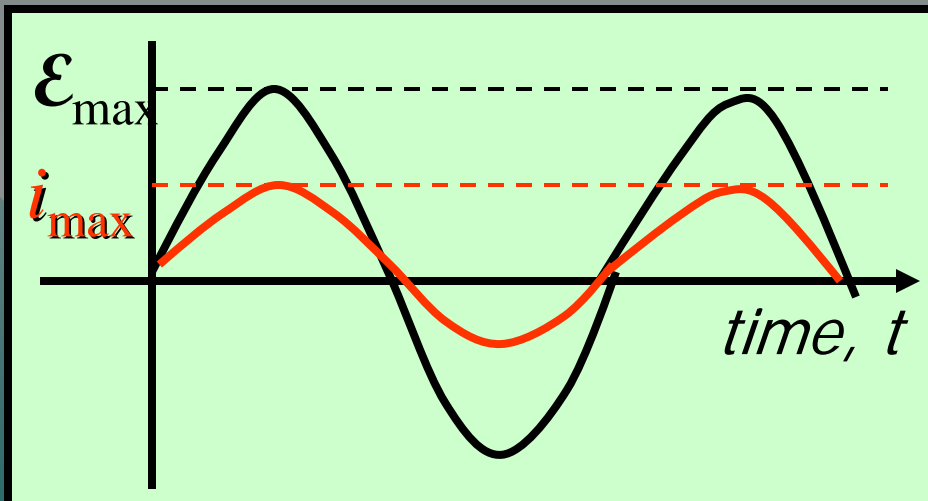

Rotating Vector Description

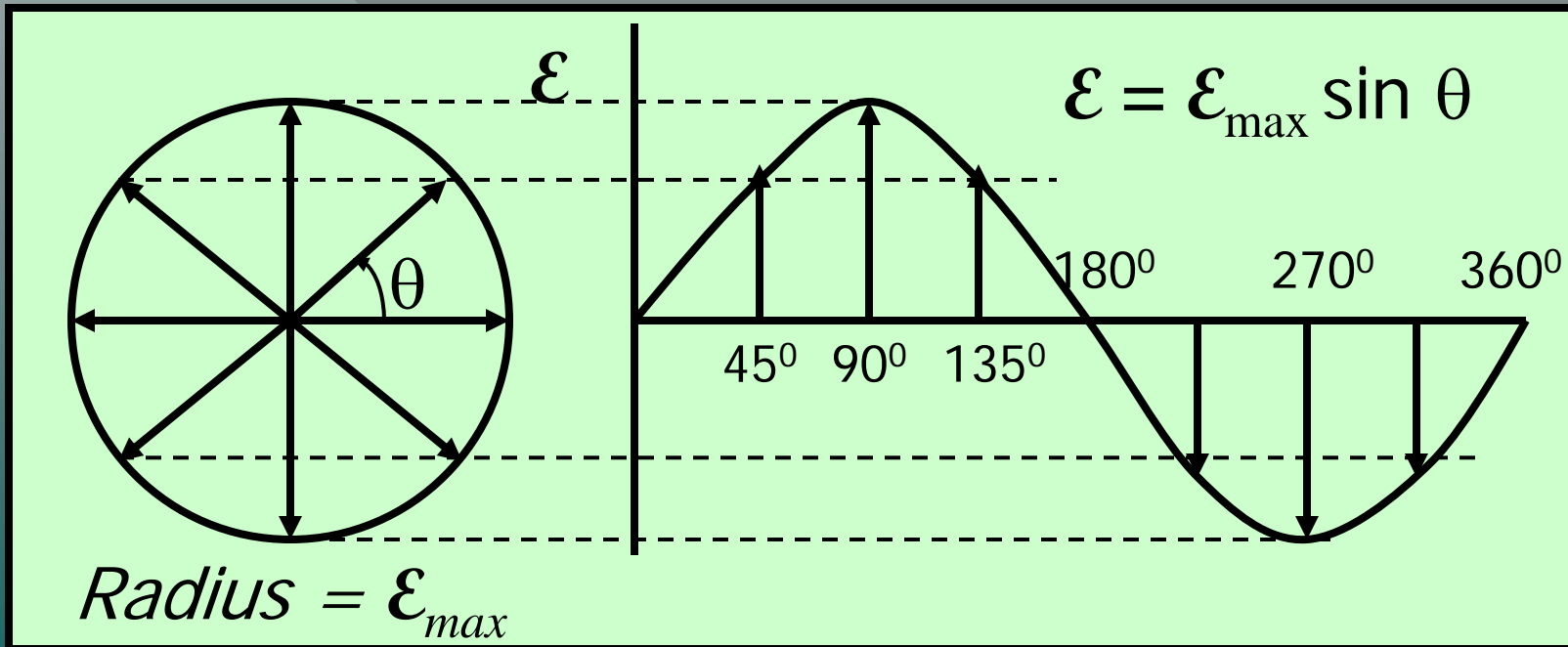The coordinate of the emf at any instant is the value of $\mathcal{E}_{\max} \sin \theta$. Observe for incremental angles in steps of 45° . Same is true for i .




Effective AC Current

The average current in a cycle is zero—half + and half -.

But energy is expended, regardless of direction. So the “**root-mean-square**” value is useful.

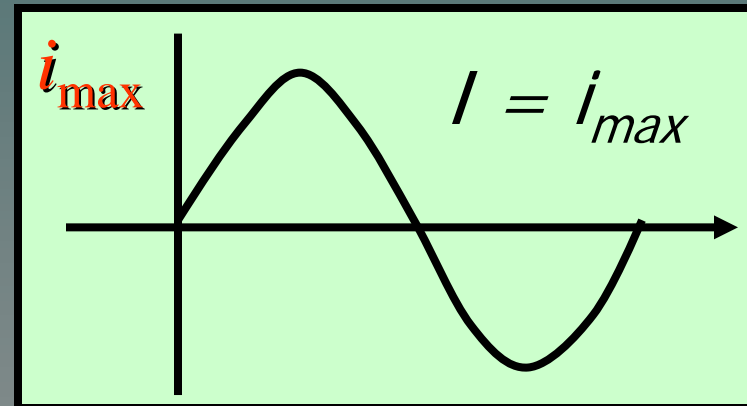The **rms** value I_{rms} is sometimes called the **effective** current I_{eff} :



$$I_{rms} = \sqrt{\frac{I^2}{2}} = \frac{I}{0.707}$$

The effective ac current:

$$i_{eff} = 0.707 i_{max}$$

AC Definitions

One **effective ampere** is that ac current for which the power is the same as for one ampere of dc current.

$$\text{Effective current: } i_{eff} = 0.707 i_{max}$$

One **effective volt** is that ac voltage that gives an effective ampere through a resistance of one ohm.

$$\text{Effective voltage: } V_{eff} = 0.707 V_{max}$$

Example 1: For a particular device, the house ac voltage is **120-V** and the ac current is **10 A**. What are their **maximum** values?

$$i_{eff} = 0.707 i_{max}$$

$$i_{max} = \frac{i_{eff}}{0.707} = \frac{10 \text{ A}}{0.707}$$

$$i_{max} = 14.14 \text{ A}$$



$$V_{eff} = 0.707 V_{max}$$

$$V_{max} = \frac{V_{eff}}{0.707} = \frac{120\text{V}}{0.707}$$

$$V_{max} = 170 \text{ V}$$

The ac voltage actually varies from **+170 V** to **-170 V** and the current from **14.1 A** to **-14.1 A**.



Pure Resistance in AC Circuits

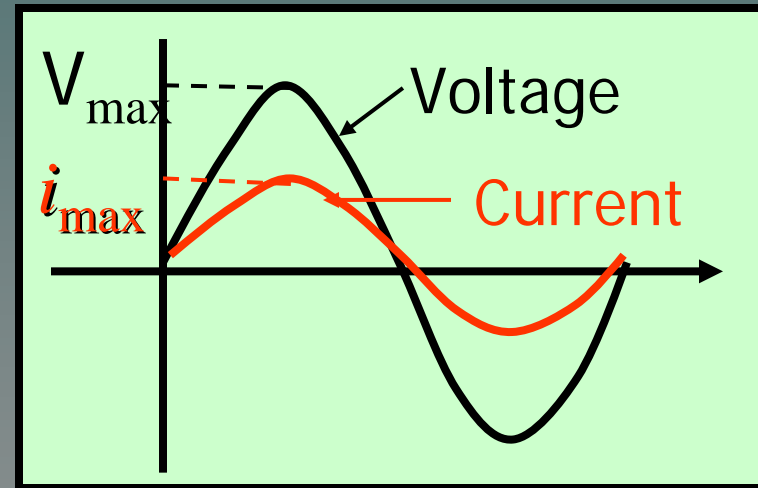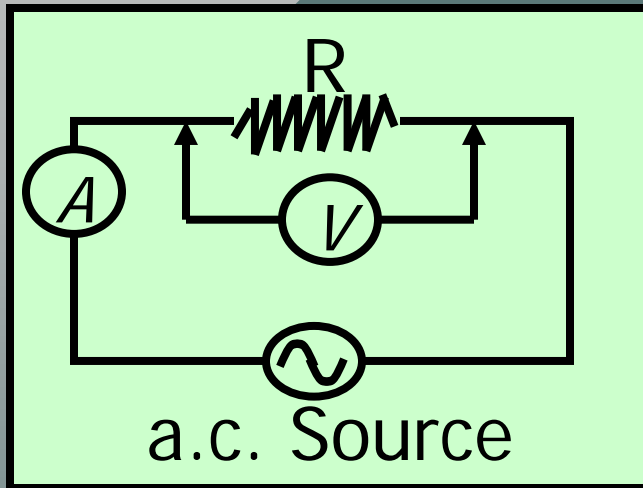

Voltage and current are in phase, and Ohm's law applies for effective currents and voltages.



$$\text{Ohm's law: } V_{\text{eff}} = i_{\text{eff}} R$$

AC and Inductors

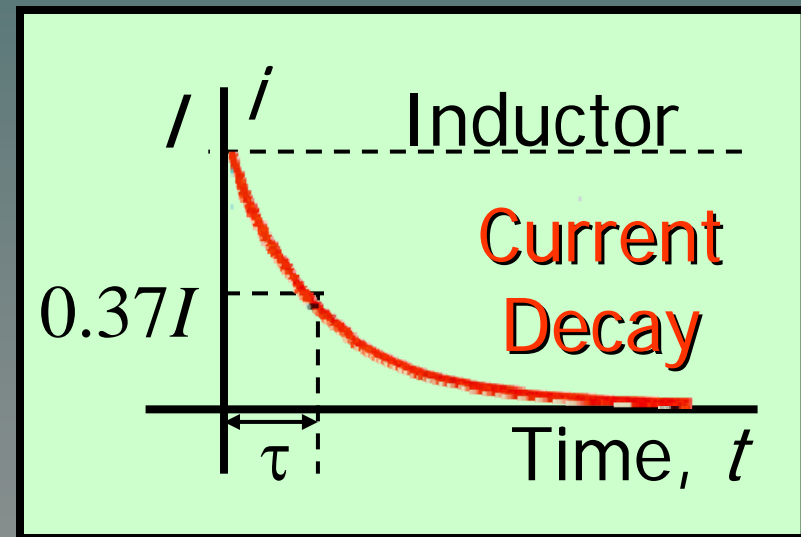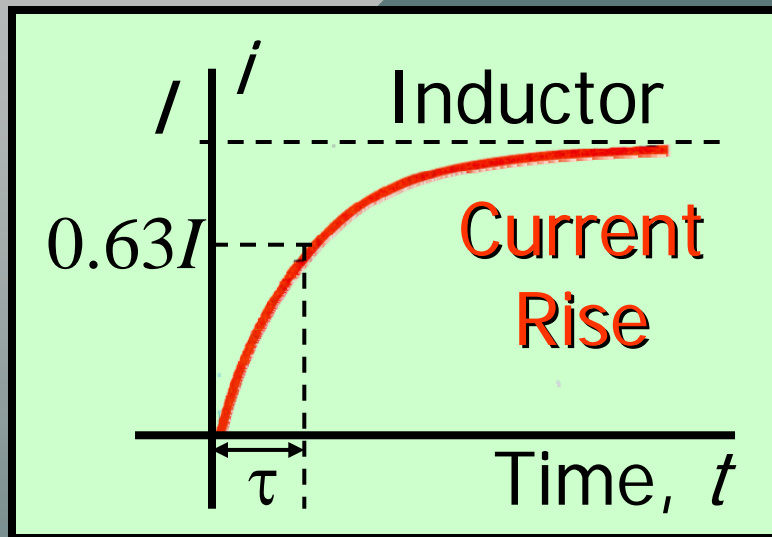

The voltage V peaks first, causing rapid rise in i current which then peaks as the emf goes to zero. Voltage **leads** (peaks before) the current by 90° . Voltage and current are out of phase.

A Pure Inductor in AC Circuit

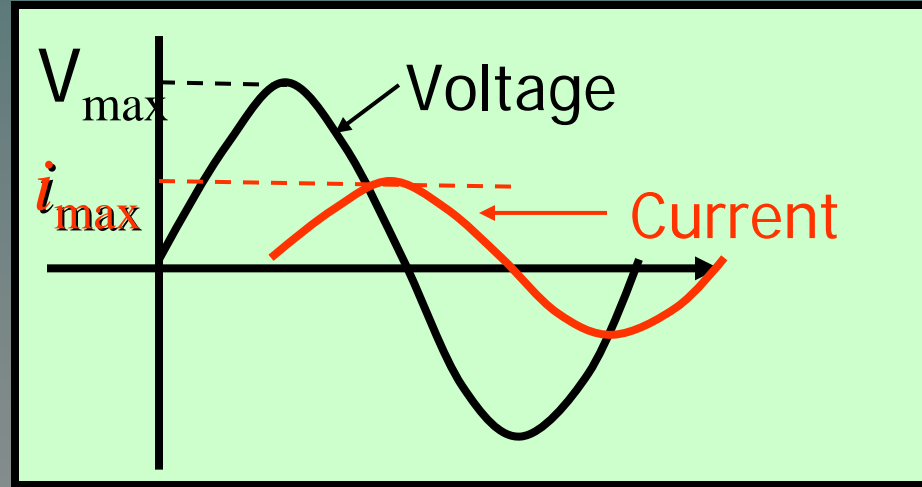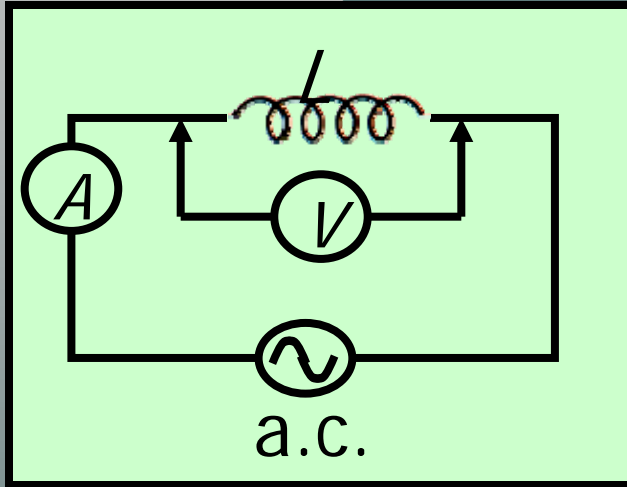


The voltage peaks 90° before the current peaks. One builds as the other falls and vice versa.

The **reactance** may be defined as the **nonresistive opposition** to the flow of ac current.

Inductive Reactance

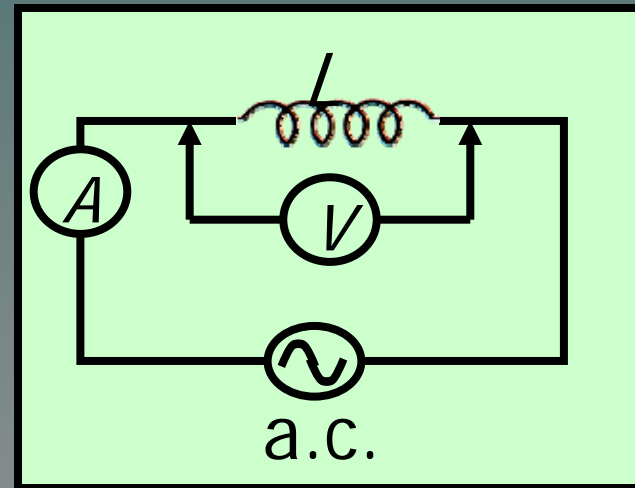
The **back emf** induced by a changing current provides opposition to current, called **inductive reactance** X_L .



Such losses are **temporary**, however, since the current **changes direction**, periodically re-supplying energy so that no net power is lost in one cycle.

Inductive reactance X_L is a function of both the **inductance** and the **frequency** of the ac current.

Calculating Inductive Reactance

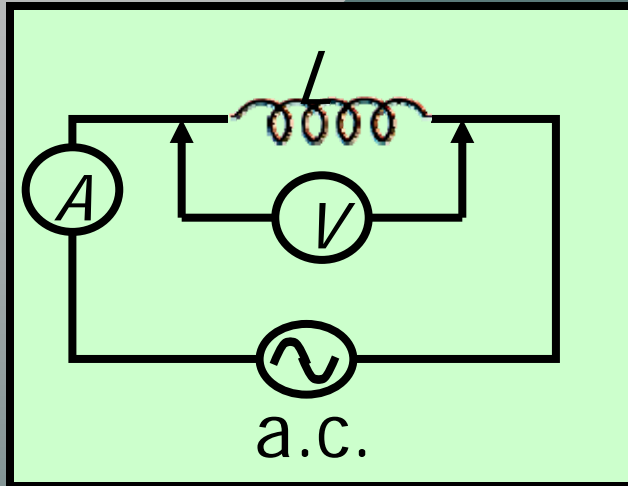

Inductive Reactance:

$$X_L = 2\pi fL \quad \text{Unit is the } \Omega$$

$$\text{Ohm's law: } V_L = iX_L$$

The **voltage** reading V in the above circuit at the instant the **ac** current is i can be found from the **inductance** in H and the **frequency** in Hz.

$$V_L = i(2\pi fL)$$


$$\text{Ohm's law: } V_L = i_{eff}X_L$$

Example 2: A coil having an inductance of **0.6 H** is connected to a **120-V, 60 Hz** ac source. Neglecting resistance, what is the effective current through the coil?

Reactance: $X_L = 2\pi fL$

$$X_L = 2\pi(60 \text{ Hz})(0.6 \text{ H})$$



$$X_L = 226 \Omega$$

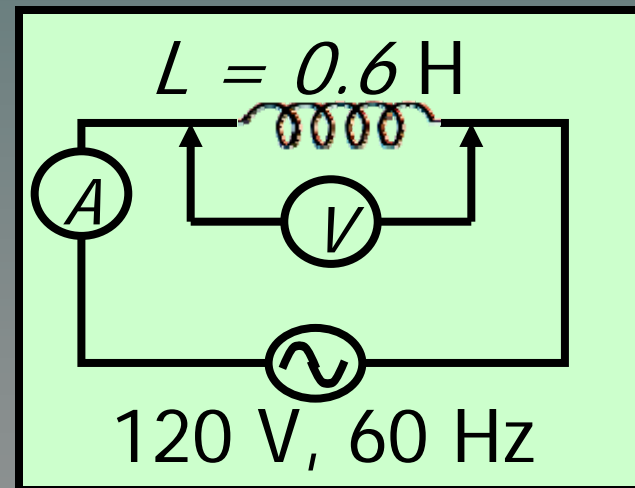

$$i_{eff} = 0.531 \text{ A}$$



Show that the peak current is $I_{max} = 0.750 \text{ A}$

AC and Capacitance

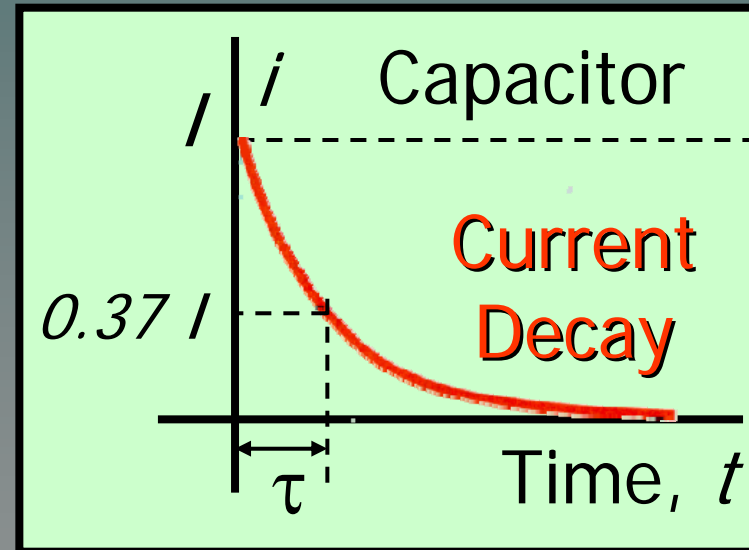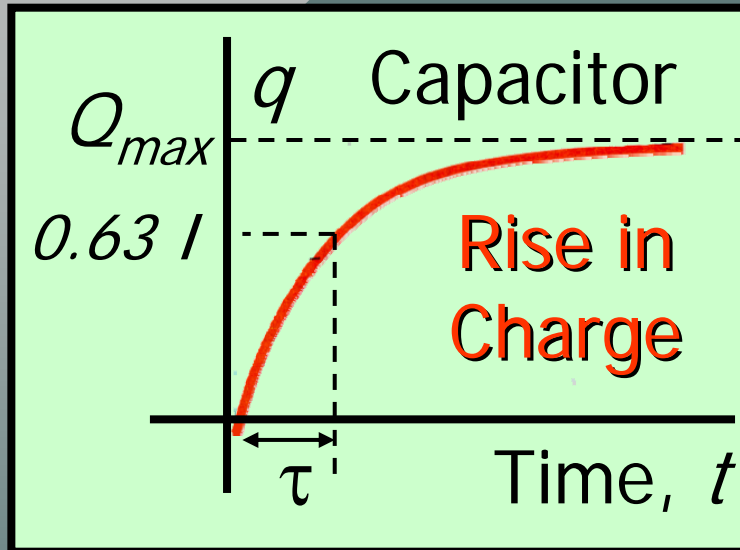

The voltage V peaks $\frac{1}{4}$ of a cycle after the current i reaches its maximum. The voltage **lags** the current. **Current i and V out of phase.**

A Pure Capacitor in AC Circuit

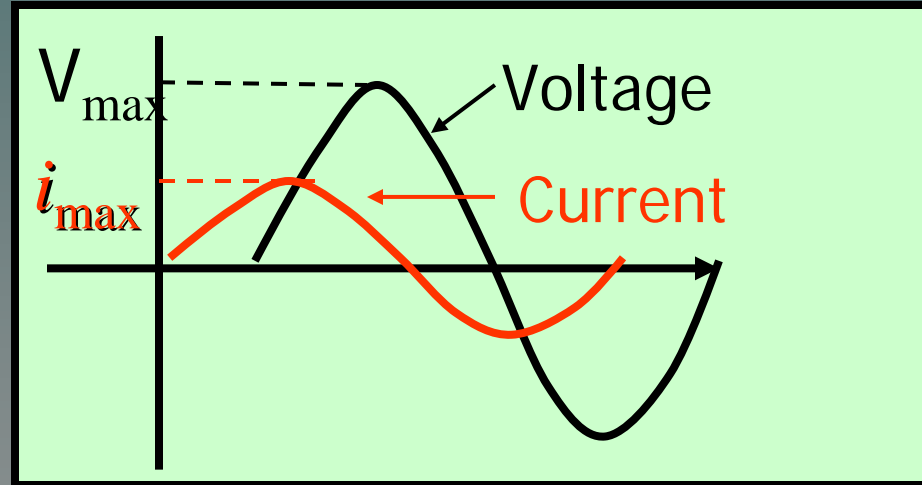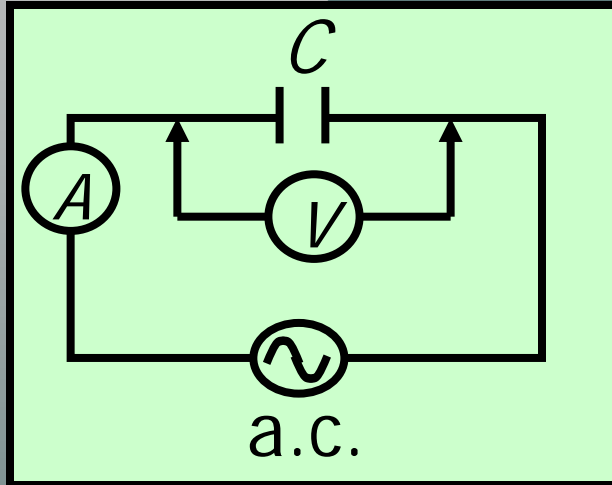


The voltage peaks 90° **after** the current peaks. One builds as the other falls and vice versa.

The diminishing current i builds charge on C which increases the **back emf** of V_C .

Capacitive Reactance

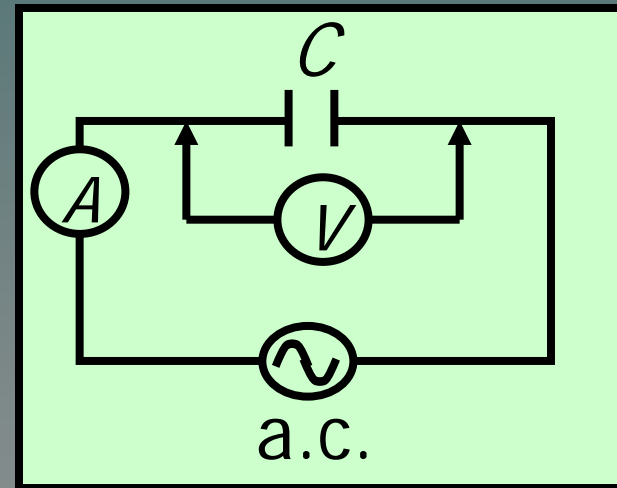
Energy gains and losses are also temporary for capacitors due to the constantly changing ac current.



No net power is lost in a complete cycle, even though the capacitor does provide nonresistive opposition (reactance) to the flow of ac current.

Capacitive reactance X_C is affected by both the capacitance and the frequency of the ac current.

Calculating Inductive Reactance

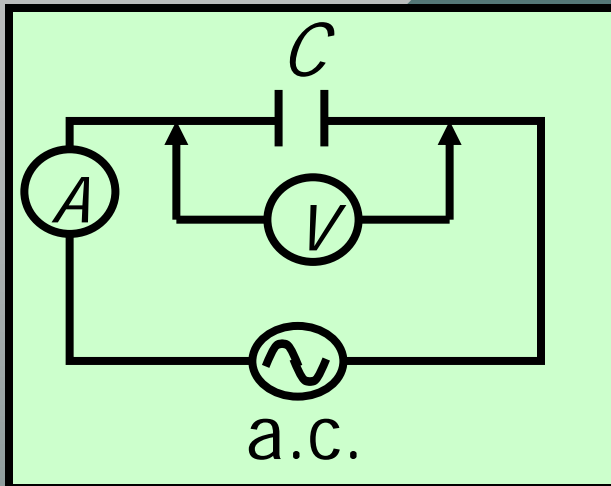

Capacitive Reactance:

$$X_C = \frac{1}{2\pi fC} \quad \text{Unit is the } \Omega$$

Ohm's law: $V_C = iX_C$

The **voltage** reading V in the above circuit at the instant the **ac** current is i can be found from the **inductance** in **F** and the **frequency** in **Hz**.

$$V_L = \frac{i}{2\pi fL}$$

Ohm's law: $V_C = i_{eff} X_C$


Example 3: A 2- μF capacitor is connected to a 120-V, 60 Hz ac source. Neglecting resistance, what is the effective current through the coil?

$$\text{Reactance: } X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{2\pi(60\text{ Hz})(2 \times 10^{-6}\text{ F})}$$

$$X_C = 1330 \Omega$$
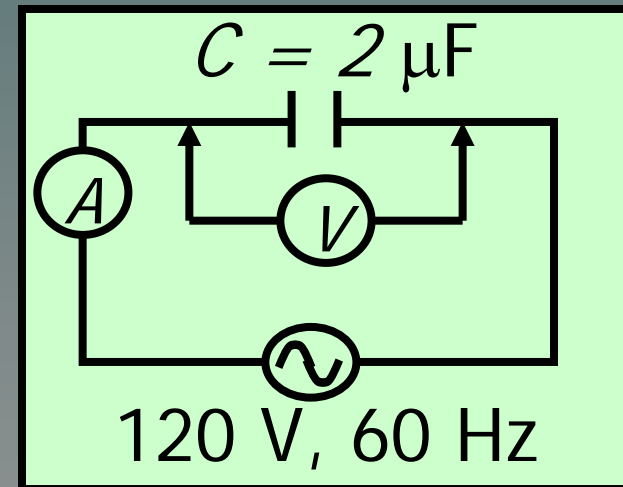
$$i_{\text{eff}} = \frac{V_{\text{eff}}}{X_C} = \frac{120\text{ V}}{1330 \Omega}$$



$$i_{\text{eff}} = 90.5 \text{ mA}$$

Show that the peak current is $i_{\text{max}} = 128 \text{ mA}$

Memory Aid for AC Elements

An **old**, but very effective, way to remember the **phase differences** for **inductors** and **capacitors** is :

" \mathcal{E} L I" the " i C \mathcal{E} " Man



Emf \mathcal{E} is **before** current i in inductors L ;
Emf \mathcal{E} is **after** current i in capacitors C .

Frequency and AC Circuits


Resistance R is constant and not affected by f .

Inductive reactance X_L varies directly with frequency as expected since $\mathcal{E} \propto \Delta i / \Delta t$.


$$X_L = 2\pi fL$$

$$X_C = \frac{1}{2\pi fC}$$

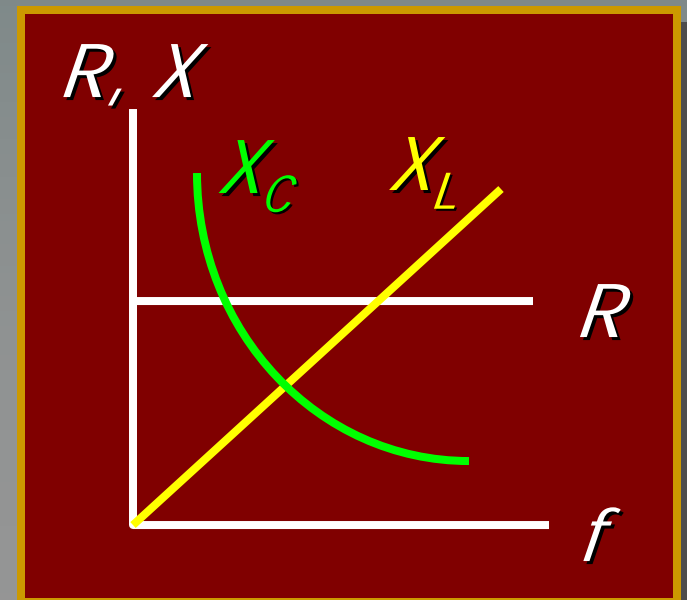Capacitive reactance X_C varies inversely with f since rapid ac allows little time for charge to build up on capacitors.




Series LRC Circuits

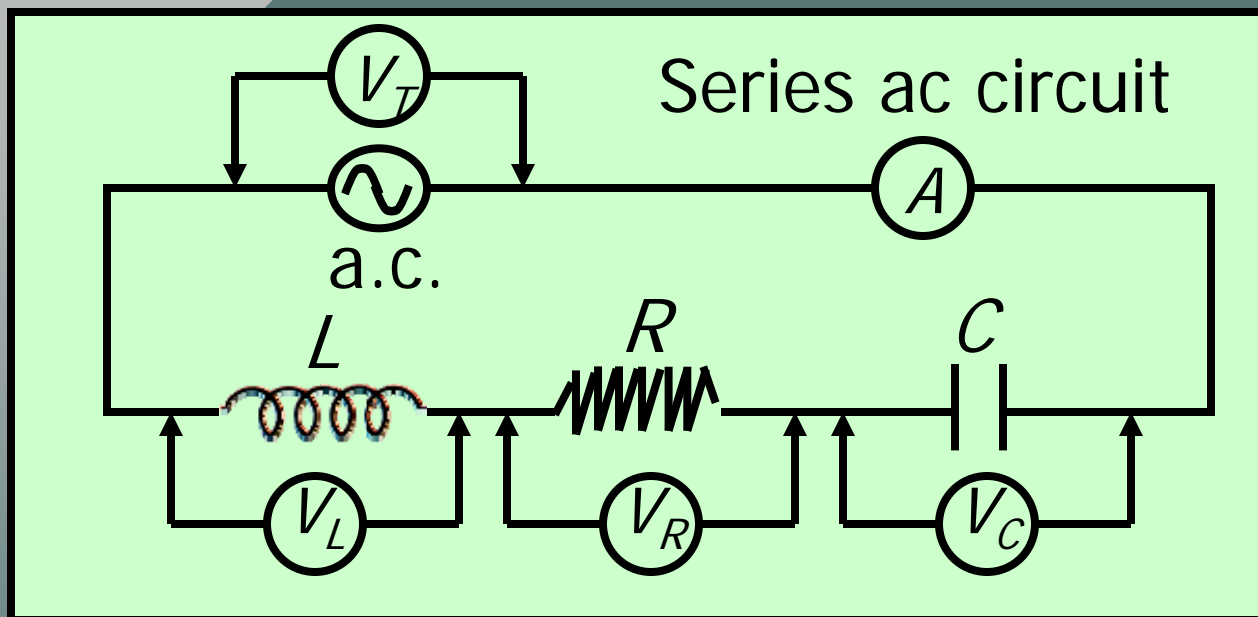

Consider an inductor L , a capacitor C , and a resistor R all connected in series with an ac source. The instantaneous current and voltages can be measured with meters.

Phase in a Series AC Circuit

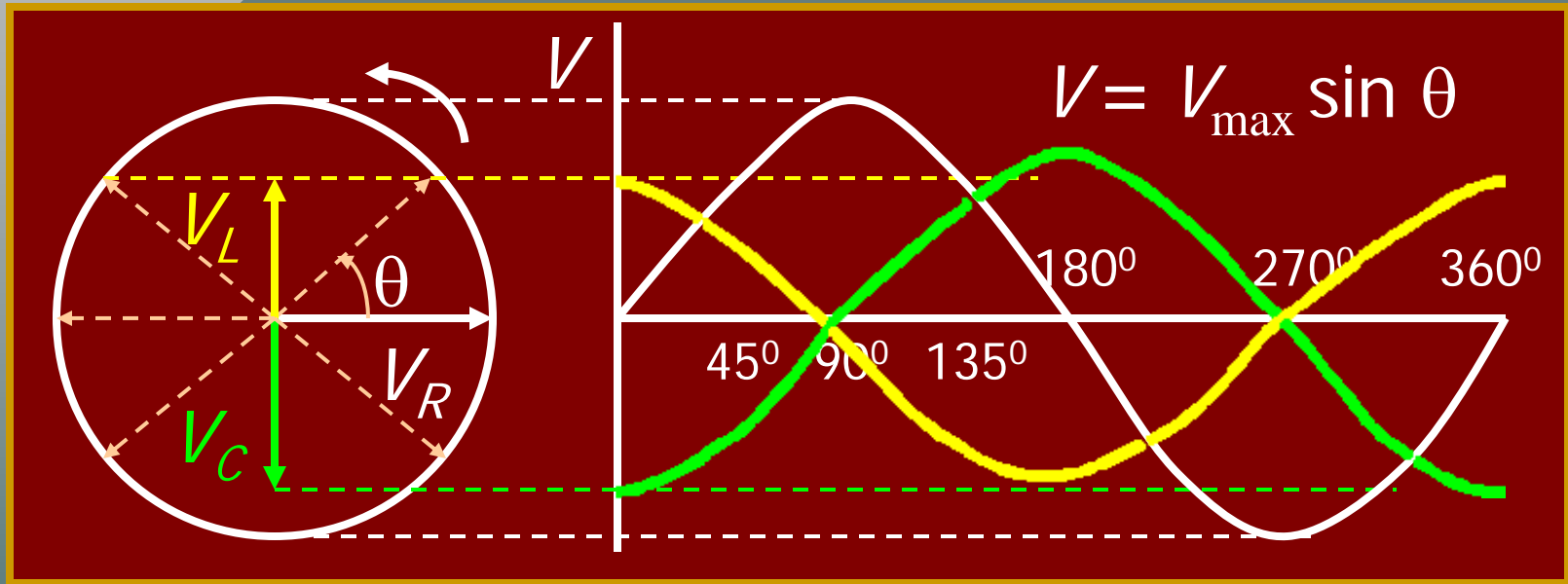
The voltage **leads** current in an inductor and **lags** current in a capacitor. **In phase** for resistance R .



Rotating **phasor diagram** generates voltage waves for each element R , L , and C showing phase relations. Current i is always **in phase** with V_R .


Phasors and Voltage

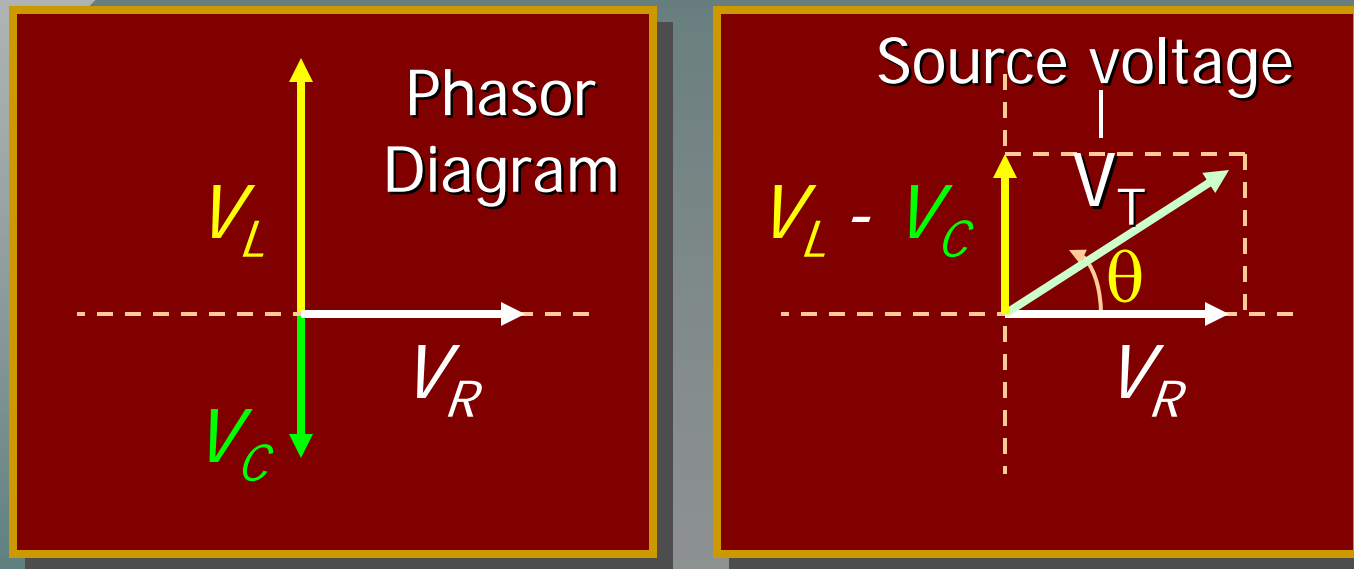At time $t = 0$, suppose we read V_L , V_R and V_C for an ac series circuit. What is the source voltage V_T ?



We handle phase differences by finding the **vector sum** of these readings. $V_T = \sum V_i$. The angle θ is the **phase angle** for the ac circuit.

Calculating Total Source Voltage

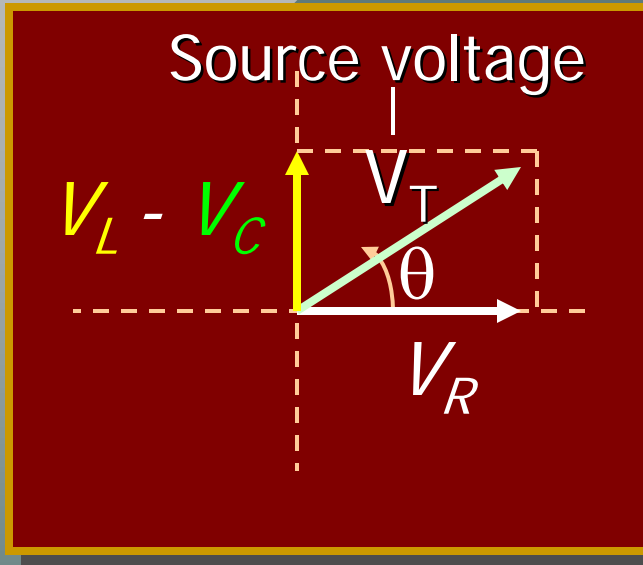

Treating as vectors, we find:

$$V_T = \sqrt{V_R^2 + (V_L - V_C)^2}$$


$$\tan \phi = \frac{V_L - V_C}{V_R}$$

Now recall that: $V_R = iR$; $V_L = iX_L$; and $V_C = iV_C$

Substitution into the above voltage equation gives:

$$V_T = i\sqrt{R^2 + (X_L - X_C)^2}$$

Impedance in an AC Circuit

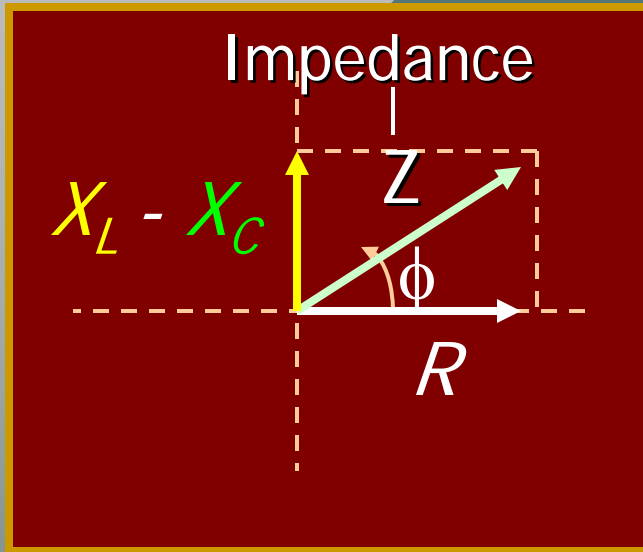

$$V_T = i\sqrt{R^2 + (X_L - X_C)^2}$$

Impedance Z is defined:

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Ohm's law for ac current and impedance:

$$V_T = iZ \quad \text{or} \quad i = \frac{V_T}{Z}$$

The impedance is the combined opposition to ac current consisting of both resistance and reactance.

Example 3: A $60\text{-}\Omega$ resistor, a 0.5 H inductor, and an $8\text{-}\mu\text{F}$ capacitor are connected in series with a 120-V , 60 Hz ac source. Calculate the impedance for this circuit.

$$X_L = 2\pi fL \quad \text{and} \quad X_C = \frac{1}{2\pi fC}$$


$$X_L = 2\pi(60\text{Hz})(0.5\text{ H}) = 226\ \Omega$$

$$X_C = \frac{1}{2\pi(60\text{Hz})(8 \times 10^{-6}\text{F})} = 332\ \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(60\ \Omega)^2 + (226\ \Omega - 332\ \Omega)^2}$$

Thus, the impedance is:

$$Z = 122\ \Omega$$

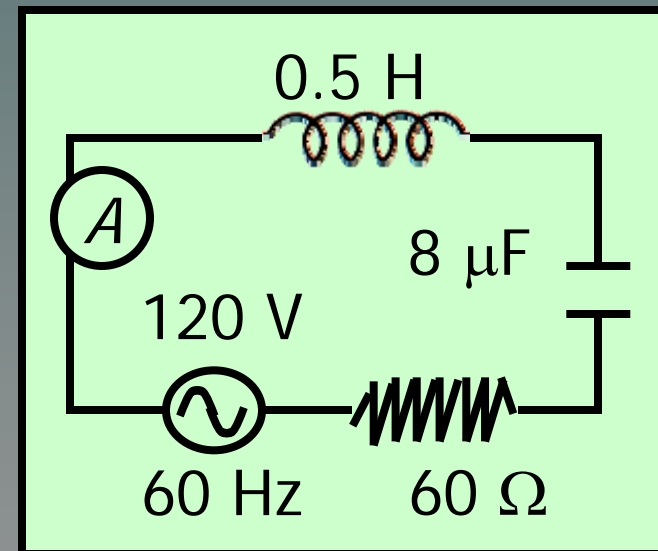


Example 4: Find the effective current and the phase angle for the previous example.


$$X_L = 226 \Omega; X_C = 332 \Omega; R = 60 \Omega; Z = 122 \Omega$$

$$i_{eff} = \frac{V_T}{Z} = \frac{120 \text{ V}}{122 \Omega}$$

$$i_{eff} = 0.985 \text{ A}$$

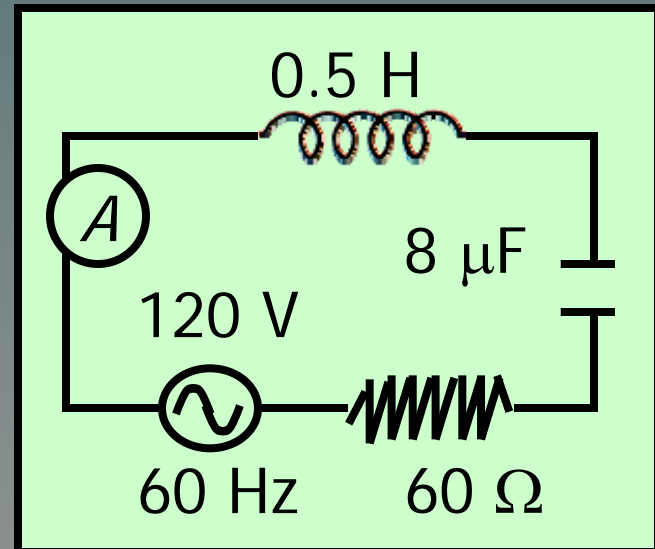

Next we find the **phase angle**:

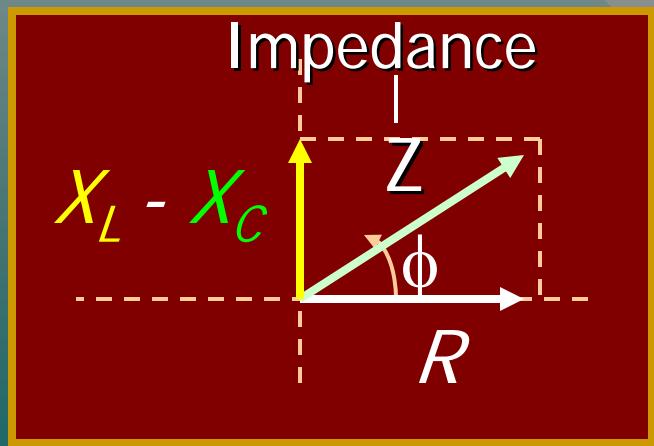


$$X_L - X_C = 226 - 332 = -106 \Omega$$

$$R = 60 \Omega$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

Continued . . .

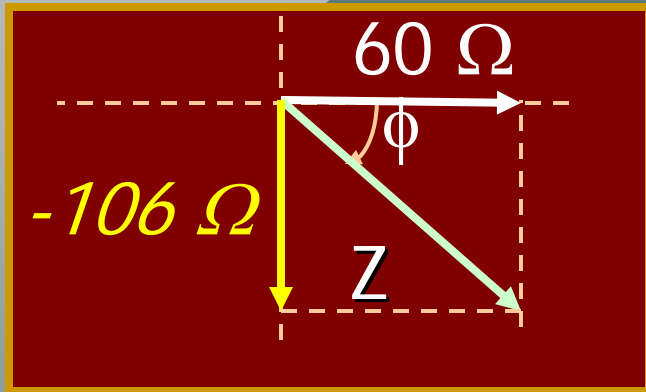Example 4 (Cont.): Find the **phase angle ϕ** for the previous example.



$$X_L - X_C = 226 - 332 = -106 \Omega$$

$$R = 60 \Omega$$

$$\tan \phi = \frac{X_L - X_C}{R}$$


$$\tan \phi = \frac{-106 \Omega}{60 \Omega}$$

$$\phi = -60.5^\circ$$

The **negative** phase angle means that the ac voltage **lags** the current by 60.5° . This is known as a **capacitive** circuit.

Resonant Frequency

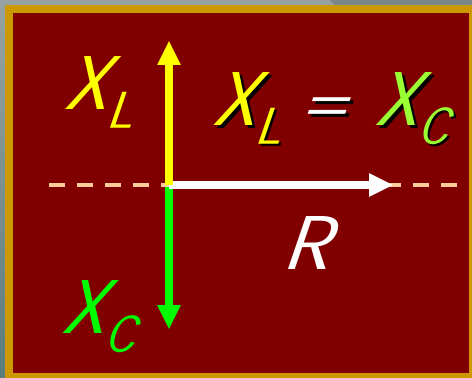Because **inductance** causes the voltage to **lead** the current and **capacitance** causes it to **lag** the current, they tend to **cancel** each other out.



Resonance (Maximum Power) occurs when $X_L = X_C$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

Resonant f_r
 $X_L = X_C \rightarrow$

$$2\pi fL = \frac{1}{2\pi fC}$$


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Example 5: Find the resonant frequency for the previous circuit example: $L = .5 \text{ H}$, $C = 8 \mu\text{F}$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{(0.5\text{H})(8 \times 10^{-6}\text{F})}}$$

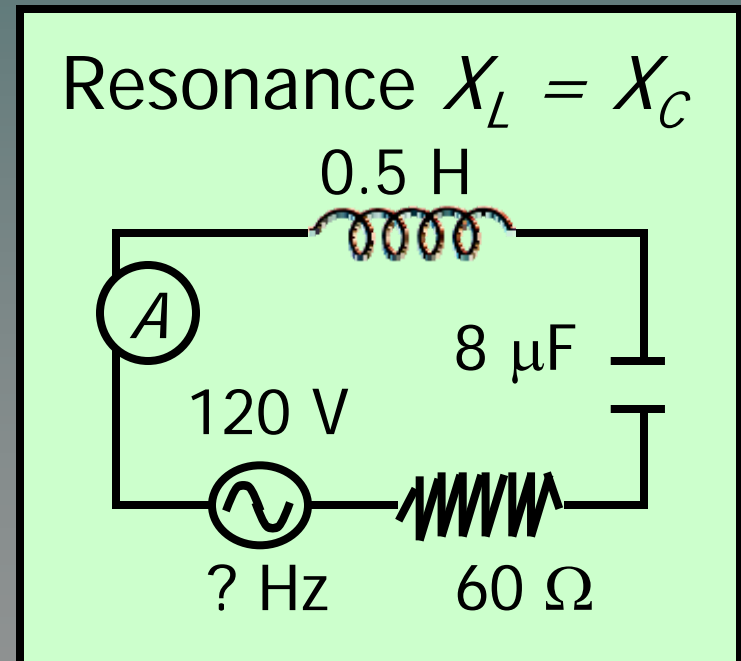
$$\text{Resonant } f_r = 79.6 \text{ Hz}$$



At resonant frequency, there is zero reactance (**only resistance**) and the circuit has a phase angle of zero.

Power in an AC Circuit

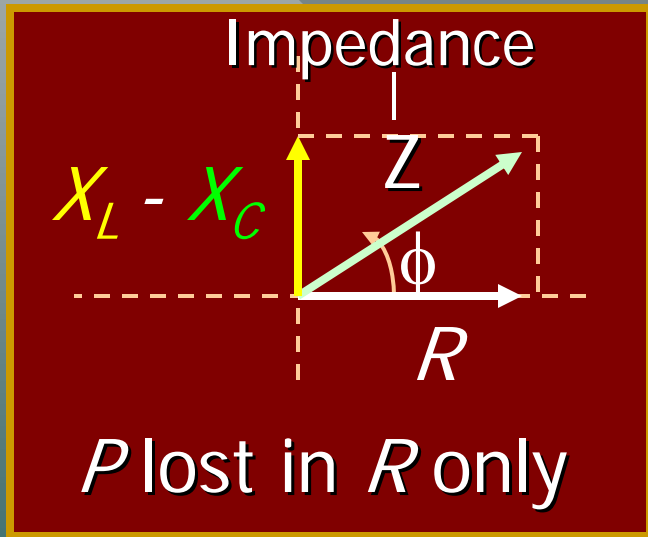No power is consumed by inductance or capacitance. Thus power is a function of the component of the impedance along resistance:



In terms of ac voltage:

$$P = iV \cos \phi$$

In terms of the resistance R :

$$P = i^2 R$$

The fraction $\cos \phi$ is known as the **power factor**.


Example 6: What is the average power loss for the previous example: $V = 120 \text{ V}$, $\phi = -60.5^\circ$, $i = 90.5 \text{ A}$, and $R = 60 \Omega$.

$$P = I^2 R = (0.0905 \text{ A})^2 (60 \Omega)$$

$$\text{Average } P = 0.491 \text{ W}$$

The power factor is: $\text{Cos } 60.5^\circ$
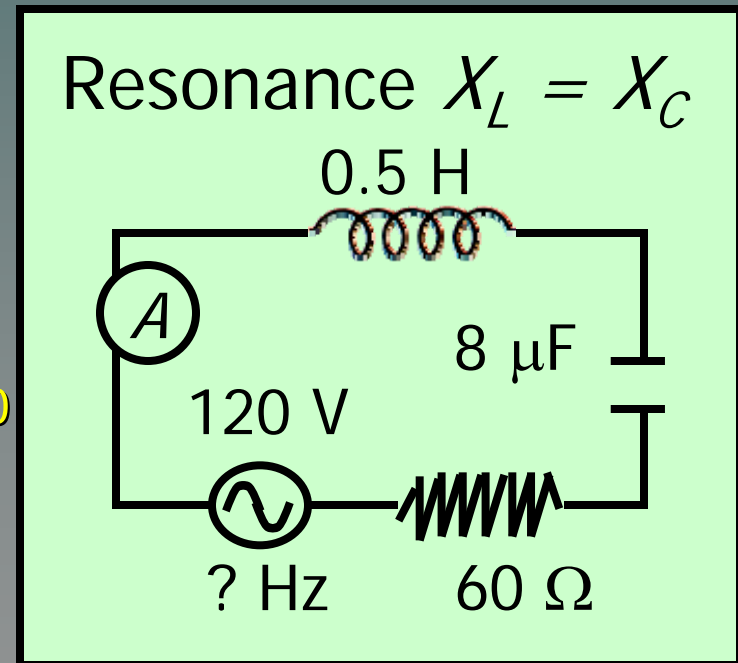
$$\text{Cos } \phi = 0.492 \text{ or } 49.2\%$$




The **higher** the power factor, the more **efficient** is the circuit in its use of ac power.

The Transformer

A **transformer** is a device that uses induction and ac current to step voltages up or down.

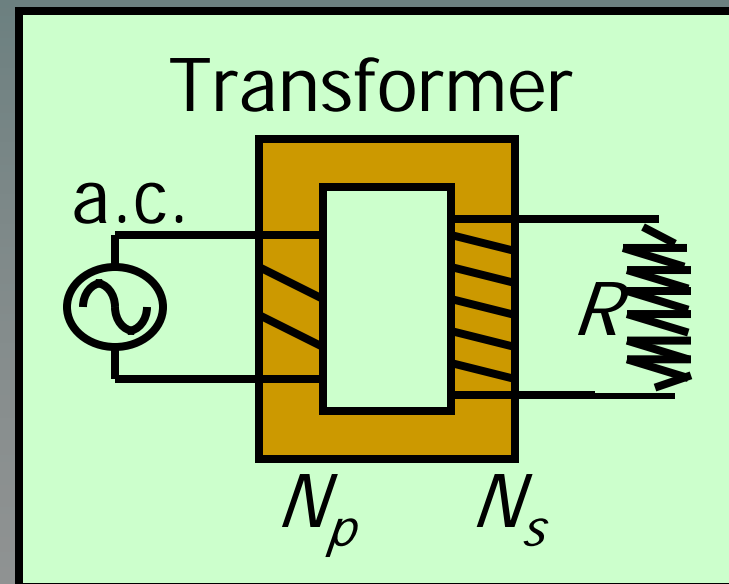An ac source of emf \mathcal{E}_p is connected to primary coil with N_p turns. Secondary has N_s turns and emf of \mathcal{E}_s .




Induced
emf's are:

$$\mathcal{E}_P = -N_P \frac{\Delta\Phi}{\Delta t}$$

$$\mathcal{E}_S = -N_S \frac{\Delta\Phi}{\Delta t}$$

Transformers (Continued):

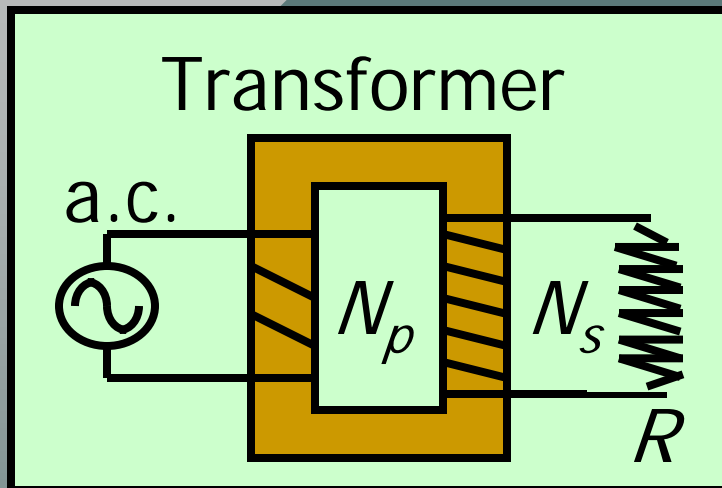

$$\mathcal{E}_P = -N_P \frac{\Delta\Phi}{\Delta t}$$

$$\mathcal{E}_S = -N_S \frac{\Delta\Phi}{\Delta t}$$

Recognizing that $\Delta\phi/\Delta t$ is the same in each coil, we divide first relation by second and obtain:

The transformer equation:


$$\frac{\mathcal{E}_P}{\mathcal{E}_S} = \frac{N_P}{N_S}$$

Example 7: A generator produces 10 A at 600 V. The primary coil in a transformer has 20 turns. How many secondary turns are needed to step up the voltage to 2400 V?

Applying the transformer equation:

$$\frac{V_P}{V_S} = \frac{N_P}{N_S}$$
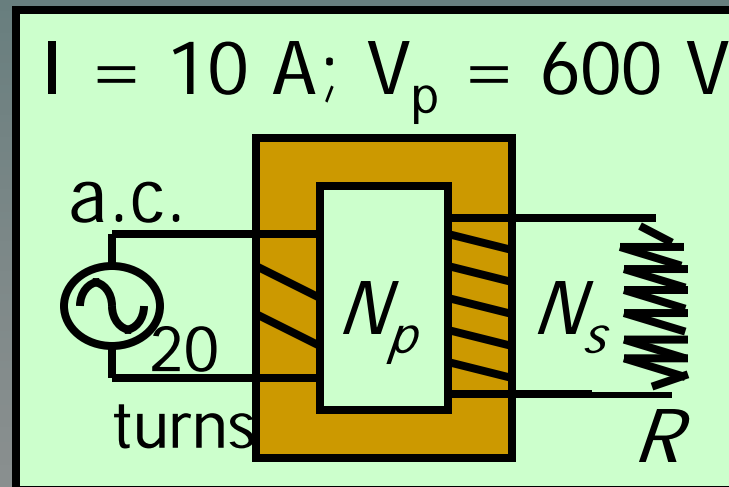
$$N_S = \frac{N_P V_S}{V_P} = \frac{(20)(2400 \text{ V})}{600 \text{ V}}$$




$$N_S = 80 \text{ turns}$$

This is a **step-up transformer**; reversing coils will make it a step-down transformer.

Transformer Efficiency

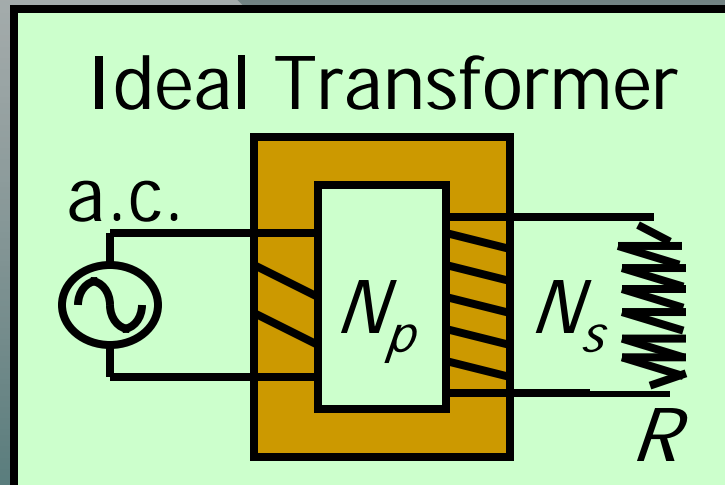There is no power gain in stepping up the voltage since voltage is increased by reducing current. In an ideal transformer with no internal losses:



An ideal transformer:

$$\mathcal{E}_P i_P = \mathcal{E}_S i_S \quad \text{or} \quad \frac{i_P}{i_S} = \frac{\mathcal{E}_S}{\mathcal{E}_P}$$


The above equation assumes no internal energy losses due to heat or flux changes. **Actual efficiencies** are usually between **90 and 100%**.

Example 7: The transformer in **Ex. 6** is connected to a power line whose resistance is **12 Ω**. How much of the power is lost in the transmission line?

$$V_S = 2400 \text{ V}$$

$$\mathcal{E}_P i_P = \mathcal{E}_S i_S \quad i_S = \frac{\mathcal{E}_P i_P}{\mathcal{E}_S}$$
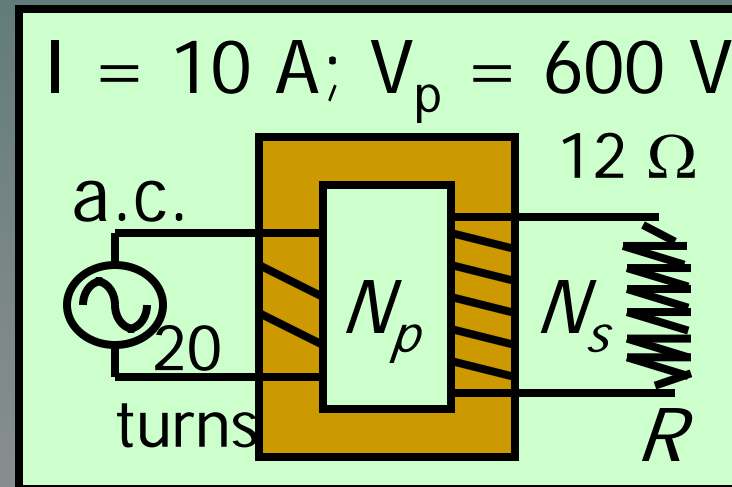
$$i_S = \frac{(600 \text{ V})(10 \text{ A})}{2400 \text{ V}} = 2.50 \text{ A}$$



$$P_{lost} = I^2 R = (2.50 \text{ A})^2 (12 \Omega) \quad P_{lost} = 75.0 \text{ W}$$

$$P_{in} = (600 \text{ V})(10 \text{ A}) = 6000 \text{ W}$$

$$\% \text{Power Lost} = (75 \text{ W} / 6000 \text{ W})(100\%) = 1.25\%$$

Summary

Effective current: $i_{eff} = 0.707 i_{max}$

Effective voltage: $V_{eff} = 0.707 V_{max}$

Inductive Reactance:

$$X_L = 2\pi fL \quad \text{Unit is the } \Omega$$

$$\text{Ohm's law: } V_L = iX_L$$

Capacitive Reactance:

$$X_C = \frac{1}{2\pi fC} \quad \text{Unit is the } \Omega$$

$$\text{Ohm's law: } V_C = iX_C$$

Summary (Cont.)

$$V_T = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$V_T = iZ \quad \text{or} \quad i = \frac{V_T}{Z}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

Summary (Cont.)

Power in AC Circuits:

In terms of ac voltage: In terms of the resistance R:

$$P = iV \cos \phi$$

$$P = i^2 R$$

Transformers:

$$\frac{\mathcal{E}_P}{\mathcal{E}_S} = \frac{N_P}{N_S} \quad \mathcal{E}_P i_P = \mathcal{E}_S i_S$$

CONCLUSION: Chapter 32A AC Circuits

